



**JARAMOGI OGINGA ODINGA UNIVERSITY OF SCIENCE AND TECHNOLOGY**  
**SCHOOL OF BIOLOGICAL, PHYSICAL, MATHEMATICS AND ACTUARIAL**  
**SCIENCES**

**UNIVERSITY EXAMINATION FOR THE DEGREE OF BACHELOR OF EDUCATION**  
**(SCIENCE)**

**MAIN**

**SPECIAL RESITS EXAMINATIONS FEB 2022**

---

**COURSE CODE: SPH 307**

**COURSE TITLE: INTRODUCTION TO DIGITAL ELECTRONICS**

**EXAM VENUE:**

**STREAM: EDUCATION**

**DATE:**

**EXAM SESSION:**

**TIME: 2:00 HRS**

---

**Instructions:**

- 1. Answer question 1 (Compulsory) and ANY other 2 questions.**
- 2. Candidates are advised not to write on the question paper.**
- 3. Candidates must hand in their answer booklets to the invigilator while in the examination room.**

### QUESTION ONE (30 MARKS)

- a. Define the term doping as used in semiconductor theory [2 mark]
- b. Distinguish between extrinsic and intrinsic semiconductors [2 marks]
- c. Explain the basic working principle of a transistor [4 marks]
- d. With the aid of a well labelled diagram, explain the working mechanism of an operational amplifier [4 marks]
- e. An NPN Transistor has a DC current gain,  $\beta$ , value of 200. Calculate the base current  $I_b$  required to switch a resistive load of 4mA. [3 marks]
- f. An NPN Transistor has a DC base bias voltage,  $V_b$  of 10v and an input base resistor,  $R_b$  of 100k $\Omega$ . What will be the value of the base current into the transistor. [3 marks]
- g. Draw a fully well labeled Output Characteristics Curves for a Typical Bipolar Transistor [4 marks]
- h. Define the term oscillator and give any three of its applications [4 marks]
- i. Write down the steps involved in analyzing an OP-Amp circuit [4 marks]

### QUESTION TWO (20 MARKS)

- a. With focus to band theory of solids, distinguish between conductors, semiconductors and solids [8 marks]
- b. Using well illustrated bonding diagrams, explain the formation of N-type and P-type semiconductors [6 marks]
- c. Draw the Voltage-Current characteristics curve of PN junction diode both in reverse and forward biasing modes. With focus to charge transport, explain the shape of the curve [6 marks]

### QUESTION THREE (20 MARKS)

- a. Define a transistor [2 marks]
- b. Draw the circuit diagram of NPN transistor in a common base configuration and explain its working principle [4 marks]
- c. Obtain the relation between  $\alpha$  and  $\beta$  parameters for a transistor [4 marks]
- d. Explain the working of a transistor as an amplifier [6 marks]
- e. Biasing of a transistor can make it operate in active region, saturation region and cut-off regions. With the aid of well labelled diagrams, explain the conditions of operation and application of each case. [4 marks]

### QUESTION FOUR (20 MARKS)

- a. Define an operational amplifier and draw its standard circuit [2 marks]
- b. Design an operational amplifier with negative feedback and fully explain its working principle. [3 marks]

- c. With the aid of well labelled circuit diagrams and with supportive voltage equations, explain the operation of the following types of op amps
- i) Voltage follower **[5 marks]**
  - ii) Inverting amplifier **[5 marks]**
  - iii) Differential amplifier **[5 marks]**

**QUESTION FIVE (20 MARKS)**

- a. There are two major types of oscillators, the feedback oscillator and the relaxation oscillator. Distinguish between the two. **[4 marks]**
- b. Using well labelled circuit diagrams, explain the operation of the following feedback RC oscillators
- i) Wien-bridge oscillator **[5 marks]**
  - ii) Phase-Shift oscillator **[5 marks]**
- c. One of the relaxation oscillators is the triangular- wave oscillator. Explain its working mechanism **[6 marks]**