



JARAMOGI OGINGA ODINGA UNIVERSITY OF SCENCE AND TECHNOLOGY

SCHOOL OF INFRMATICS AND INNOVATIVE SYSTEMS

COURSE CODE: IIT3226

COURSE TITLE: DIGITAL ELECTRONICS

EXAMINATIONS 2012/2013

TIME 2HRS KLC

INSTRUCTIONS:

- i. This paper contains five (5) questions.**
- ii. Question ONE is Compulsory and any other TWO questions**
- iii. Answer the questions on the booklet provided**
- iv. Mobile Phones are not allowed in exams room**

QUESTION ONE (30 Marks)- Compulsory

- a) Simplify the following Boolean expressions using De Morgan's theorem and/ or Boolean algebra
- i) $ABC + \bar{A}CD + \bar{B}CD$ (4 Marks)
 - ii) $AB + (C + \bar{B})(AB + \bar{C})$ (4 Marks)
- b) Simplify the following Boolean equation using Karnaugh map.
 $F(X,Y,Z) = (1,3,4,5,6)$ (4 Marks)
- c) Express the Boolean function depicted in the K-Map shown below as Boolean equation in Product- of- Sum form (4 Marks)

AB				
1	1	0	1	CD
0	1	0	0	
0	0	0	0	
1	1	0	1	

- d) Compare Analog and Digital systems. Explain the advantages and disadvantages of digital systems over analog systems. (6 Marks)
- e) Explain the working of JK Flip Flop with the help of its logic diagram, characteristic equation, state table and excitation table. (8 Marks)

QUESTION TWO (20 Marks)

- a) Draw and explain the logic circuit and truth table for an Octal to Binary Encoder (6 Marks)
- b) Perform the operation of subtractions with the following binary numbers using 2 complement
 (i) 10010 - 10011 (ii) 100 - 110000 (iii) 11010 - 10000 (6 Marks)
- c) Design a combinational circuit that accepts a three bit binary number and generates an output binary number equal to the square of the input number. (5 Marks)
- d) Demonstrate by means of truth table the validity of the De Morgan's theorems for three variables of Boolean algebra (3 Marks)

QUESTION THREE (20 Marks)


- a) Implement a full adder circuit using NAND gates only, show the truth table (7 Marks)
- b) With neat sketch explain the operation of clocked RS flip (7 Marks)
- c) Perform the following decimal arithmetic calculations by first converting the given decimal numbers into their binary equivalent then using 2's complement effect the calculation. (6 Marks)
- i) 48- 72
 - ii) 524- 320

QUESTION FOUR (20 Marks)

- a) Describe the architecture of PALs with the aid of one or more illustrative diagrams. (4 Marks)
- b) Indicate clearly how a PAL device would be programmed to implement a full adder (4 Marks)
- c) Design a 3-to- 8 decoder (8 Marks)
- a) Implement Boolean expression for Ex-OR gate using NAND gates only (4Marks)

QUESTION FIVE (20 Marks)

 - a) The 1-bit full Subtractor shown below performs the binary subtraction ($P-Q-B_{in}$) where P and Q are 1-bit variables and B_{in} is a borrow input from the previous stage. It produces two outputs: the difference D and the borrow output B_{out} . The truth table describing the function of the 1-bit full Subtractor is also shown.
- Derive the Boolean equations for D and B_{out} (3 Marks)
 - Implement these equations using only NOR gates (5 Marks)



B_{in}	P	Q	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

- Draw and explain the logic circuit and truth table for an Octal to Binary Encoder. (6 Marks)
- Give classification of counters and explain any one of them (6 Marks)