



JARAMOGI OGINGA ODINGA UNIVERSITY OF SCIENCE AND TECHNOLOGY
SCHOOL OF BIOLOGICAL AND PHYSICAL SCIENCES
UNIVERSITY EXAMINATION FOR THE DEGREE OF BACHELOR OF EDUCATION
(SCIENCE)
3RD YEAR 2ND SEMESTER 2016/17
MAIN REGULAR

COURSE CODE: SCH 314

COURSE TITLE: DIGITAL ELECTRONICS

EXAM VENUE: PHY LAB

STREAM: (BED SCI)

DATE: 06/09/16

EXAM SESSION: 2.00 – 4.00 PM

TIME: 2:00HRS


Instructions:

- 1. Answer question 1 (Compulsory) in Section A and ANY other 2 questions in Section B.**
- 2. Candidates are advised not to write on the question paper.**
- 3. Candidates must hand in their answer booklets to the invigilator while in the examination room**

SECTION A

QUESTION 1

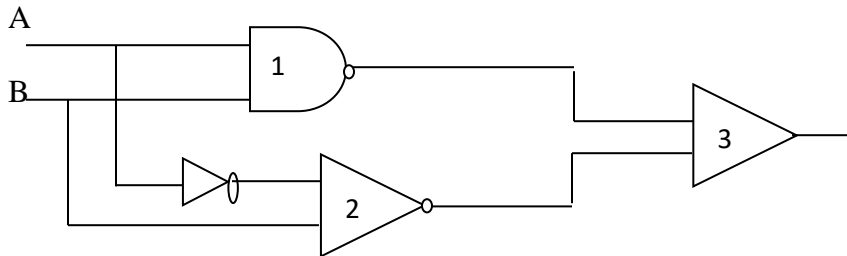- a. Draw the symbol of 4-input NOR gate and create its truth table (3 marks)
- b. Given the Boolean function $Y = [(A + B)(\overline{A + C})] + [(\overline{AC})(B + C)]$
 - i) Draw the combinational logic circuit diagram for the function. (4 marks)
 - ii) Construct its truth table (4 marks)
 - iii) From the truth table deduce its logic operation (2 marks)
- c. Find the Boolean expression for the logic circuit shown in the figure below and simplify it using Boolean algebra (4 marks)



- d. Distinguish between discrete circuits and Integrated circuits (2 marks)

(e) Define the following parameters of logic families

- i. Fan out
- ii. Propagation delay
- iii. Noise margin

(3mks)

(ii)The CMOS logic family offers some significant advantages over bipolar logic family. Name any three (3mks)

SECTION B

QUESTION 2

(a) Calculate the values of the following unknowns

(i) $(13.375)_{10} = x_2$ (3mks)

(ii) $(82.25)_{10} = Q_{16}$ (3mks)

(iii) $(00101001.0111010)_{BCD} = Z_2$ (3mks)

(a) Perform the following subtractions using 2's complement method

(i) $01000 - 01001$ (4 mks)

(ii) $01100 - 00011$ (4 mks)

(b) Using one's complement, complete the following subtractions

$11001 - 10110$ (3 mks)

QUESTION 3

- a. ICs can be classified according two distinct parameters, **the fabrication method** and **the integration scale**. Fully give the types of ICs as per these two parameters. (8 marks)
- b. Give a detailed account of the following logic families, giving their schematic diagrams.
 - i. TTL NAND gate with open collector output
 - ii. CMOS inverter (8 marks)
- c. Briefly explain the four types of TTL logic families (4marks)

QUESTION 4

- a. Simplify the Boolean expressions below using Boolean theorems (6 marks)
- b. Simplify the Boolean expressions below using Karnaugh maps (6 marks)
- c. State the DeMorgans theorems (4 marks)
- d. Use DeMorgans theorems to simplify the Boolean expression below (4 marks)

QUESTION 5

- a. One of the pilot's instructions in the manual reads: If chimney is not blocked and the house is cold and the pilot light is lit, then open the main fuel valve to start boiler.
 - i. Draw a logic circuit diagram for this instruction using a desired gate
 - ii. Write down its Boolean expression
 - iii. Draw its Truth table. (10 marks)
- b. Briefly distinguish between a digital signal and an analogue system (6 marks)
- c. Draw an analogous electrical circuit for an AND gate (4 marks)